

Chapter 2

Review of Network Parameters and Transmission Line Theory

- ❖ Review of Network Parameters
- ❖ Transmission Line Theory



Review of Network Parameters

- ❖ **Linear networks** can be completely characterized by **parameters measured** at the network ports without knowing the content of the networks
- ❖ Networks can have any number of ports.
 - ❖ Analysis of a **2-port network** is sufficient to explain the theory of network parameters

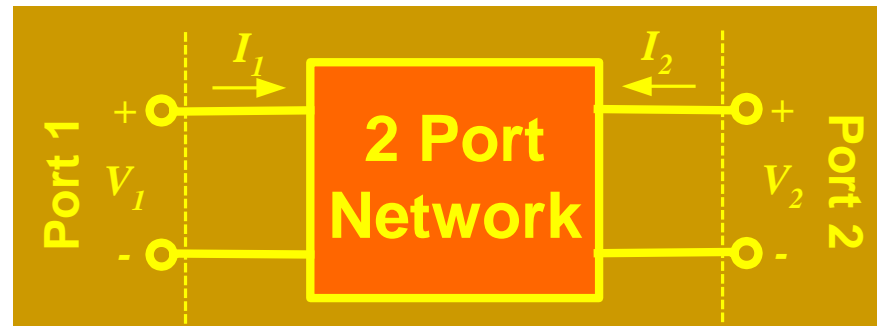


Fig. 2.1 Two port network

- ❖ The ports can be characterized with many **parameters** (**Z, Y, ABCD, S**)



Z- Parameters

- ❖ Consider the two-port network shown in Fig2.1.
- ❖ Since the network is linear, the **superposition principle** can be applied
- ❖ Assuming that it contains no independent sources, voltage V_1 and V_2 can be expressed in terms of I_1 and I_2 as follows

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

- ❖ Using the matrix representation, we can write

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \text{or} \quad [V]=[Z][I]$$



Continued

❖ Generally , for **N** port network we can express the network parameters using the **matrix** representation

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & & & \vdots \\ \vdots & & & \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix}$$

where

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_{k \neq j} = 0}$$

(Open circuit impedance)



Admittance Parameters

- ❖ Consider again the two-port network shown in Figure 2.1
- ❖ Since the network is linear, the superposition principle can be applied
- ❖ Assuming that it contains no independent sources, current I_1 and I_2 can be expressed in terms of two voltages:

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned}$$

Using the matrix representation, we can write

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \text{or} \quad [I] = [Y][V]$$



Continued

- Generally , for **N** port network we can express the network parameters using the **matrix** representation

$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1N} \\ Y_{21} & & & \vdots \\ \vdots & & & \\ Y_{N1} & Y_{N2} & \dots & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix}$$

$$[I] = [Y][V]$$

Where

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_{k \neq j} = 0}$$

(Short circuit admittance)



Transmission (ABCD) Matrix

- ❖ The transmission matrix describes the network given in Fig 2.1 above in terms of both voltage and current waves

$$\begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned}$$

or

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

- ❖ The **coefficients** can be calculated as follows:

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$



Continued

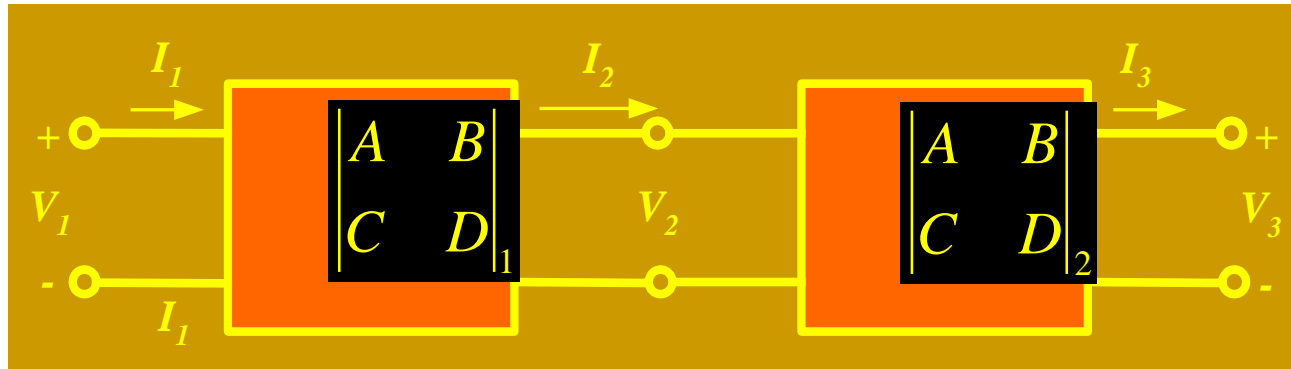- ❖ Since the **ABCD** matrix represents the ports in terms of currents and voltages, it is well suited for cascading elements




- ❖ The matrices can be mathematically cascaded by multiplication

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_1 \cdot \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$
$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_2 \cdot \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_1 \cdot \begin{bmatrix} A & B \\ C & D \end{bmatrix}_2 \cdot \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

Continued

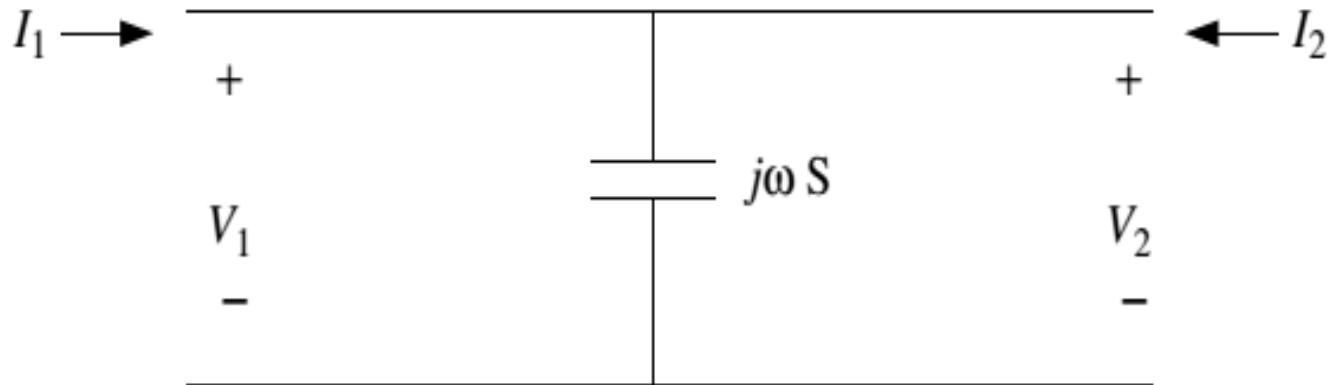Example. Determine the transmission parameters of the network shown in fig 2.3 below



Continued

SOLUTION With a source connected at port 1 while port 2 has a short circuit (so that V_2 is zero),

$$I_2 = -I_1 \quad \text{and} \quad V_1 = 0\text{V}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = 0 \Omega$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = 1$$

❖ Similarly, with a source connected at port 1 while port 2 is open (so that I_2 is zero), $V_2 = V_1$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1$$

Hence, transmission matrix of this network is

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = j\omega \quad \text{S}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ j\omega & 1 \end{bmatrix}$$



Hybrid Parameters

- ❖ Reconsider the two-port network of Figure 2.1
- ❖ Since the network is linear, **the superposition principle** can be applied
- ❖ Assuming that it contains no independent sources, voltage V_1 at port 1 can be expressed in terms of current I_1 at port 1 and voltage V_2 at port 2
- ❖ Similarly, we can write I_2 in terms of I_1 and V_2

$$\begin{aligned}V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2\end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$



Continued

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

- ❖ h_{11} = input impedance
- ❖ h_{21} = forward current gain
- ❖ h_{12} = reverse voltage gain
- ❖ h_{22} = reverse output admittance circuit
- ❖ In transistor circuit analysis, these are generally denoted by h_i , h_f , h_r , and h_o , respectively



Transmission Line Theory

- ❖ **Transmission line** is a distributed-parameter network, where **voltages** and **currents** can **vary** in **magnitude** and **phase** over the length of the line

Lumped Element Model for a Transmission Line

- ❖ **Transmission lines** usually consist of **2 parallel** conductors
- ❖ A short segment Δz of transmission line can be modeled as a lumped-element circuit.



Continued

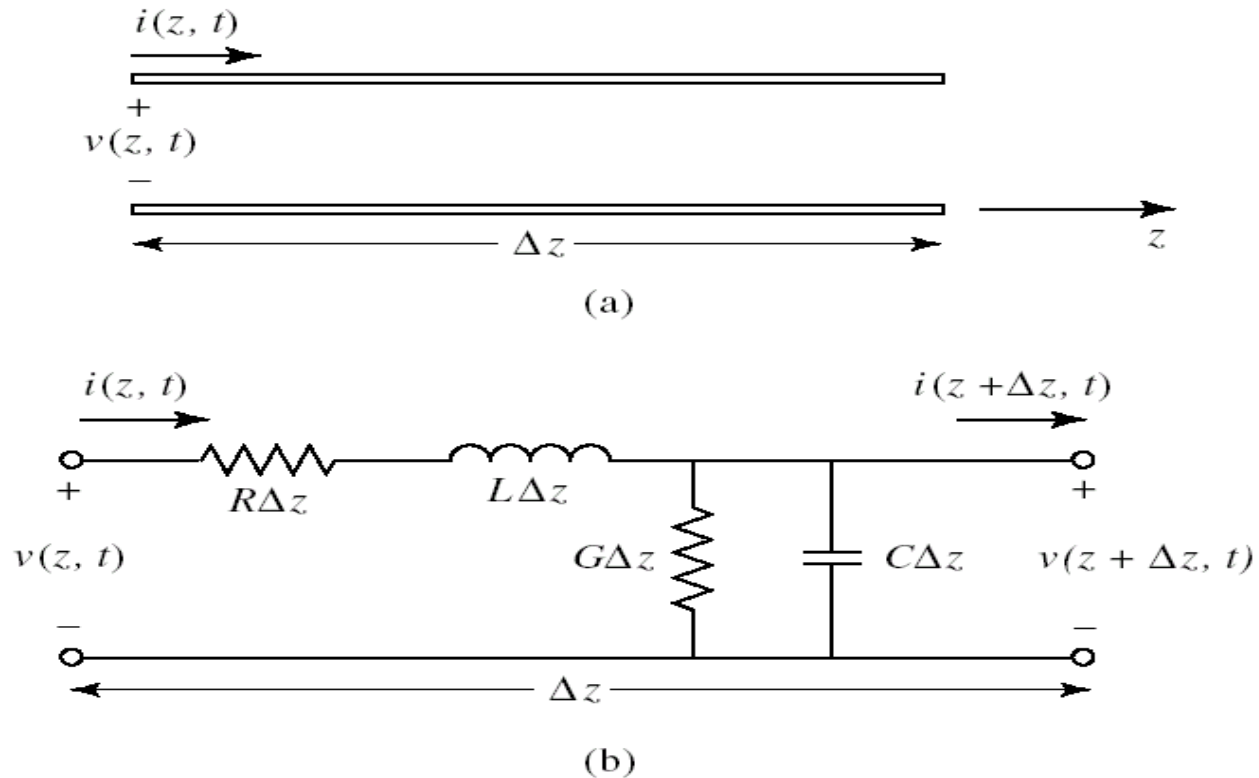


Figure 2.4 Voltage and current definitions and equivalent circuit for an incremental length of transmission line. (a) Voltage and current definitions. (b) Lumped-element equivalent circuit.

Transmission line parameters

- ❖ **R** = Series resistance per unit length for both conductors
- ❖ **L** = Series inductance per unit length for both conductors
- ❖ **G** = Shunt conductance per unit length
- ❖ **C** = Shunt capacitance per unit length
- ❖ Applying **KVL** and **KCL**,

$$v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0 \quad (2.1a)$$

$$i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0 \quad (2.1b)$$



Continued

- ❖ Dividing (2.1) by Δz and $\Delta z \rightarrow 0$,

$$\frac{\partial v(z,t)}{\partial z} = -Ri(z,t) - L \frac{\partial i(z,t)}{\partial t} \quad (2.2a)$$

$$\frac{\partial i(z,t)}{\partial z} = -Gv(z,t) - C \frac{\partial v(z,t)}{\partial t} \quad (2.2b)$$

→ Time-domain form of the transmission line, or telegrapher, equation

- ❖ For the sinusoidal steady-state condition with cosine-based phasors

$$\frac{dI(z)}{dz} = -(G + j\omega C)V(z) \quad (2.3b)$$



Wave Propagation on a Transmission Line

$$\frac{d^2V(z)}{dz^2} + \gamma^2 V(z) = 0 \quad (2.4a)$$

$$\frac{d^2I(z)}{dz^2} + \gamma^2 I(z) = 0 \quad (2.4b)$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

γ

Propagation Constant in per meter

α

Attenuation Constant in nepers per meter

β

Phase Constant in radians per meter



Continued

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}, \quad I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{+\gamma z} \quad (2.6)$$

Wave
propagation in
+z directon

Wave
propagation in
-z directon

Applying (2.3a) to the voltage of (2.6),

$$I(z) = \frac{\gamma}{R + j\omega L} \left[V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z} \right]$$



Continued

$$Z_0 = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}, (2.7) \quad \longrightarrow \quad \frac{V_0^+}{I_0^+} = Z_0 = -\frac{V_0^-}{I_0^-}$$

(2.6) can be rewritten

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z} \quad (2.8)$$

Converting the phasor voltage of (2.6) to the time domain:

$$v(z, t) = |V_0^+| \cos(\omega t - \beta z + \phi^+) e^{-\alpha z} + |V_0^-| \cos(\omega t + \beta z + \phi^-) e^{\alpha z} \quad (2.9)$$



Continue

The **wavelength** of the traveling waves:

$$\lambda = \frac{2\pi}{\beta} \quad (2.10)$$

The **phase velocity** of the wave is defined as the **speed** at which a constant **phase** point travels down the line,

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta} = \lambda f \quad (2.11)$$



Lossless Transmission Lines

❖ $R = G = 0$ gives $\gamma = \alpha + j\beta = j\omega\sqrt{LC}$ or

$$\beta = \omega\sqrt{LC}, \quad \alpha = 0 \quad (2.12)$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad (2.13)$$

❖ The general solutions for voltage and current on a lossless transmission line:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z},$$
$$I(z) = \frac{I_0^+}{Z_0} e^{-j\beta z} - I_0^- e^{j\beta z} \quad (2.14)$$



Continued

❖ The **wavelength** on the line:

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}} \quad (2.15)$$

❖ The **phase velocity** on the line:

$$v_p = \frac{\omega}{\beta} = \sqrt{\frac{1}{LC}} \quad (2.16)$$



The Terminated Lossless Transmission Lines

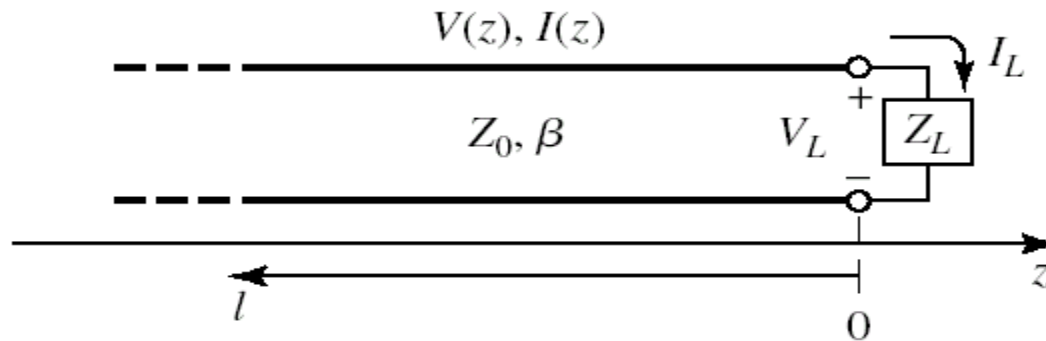


Fig 2.5 Terminated Lossless Transmission Lines

❖ The total voltage and current on the line:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z},$$
$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z} \quad (2.34)$$



Continued

❖ The **total voltage** and **current** at the load are related by the load impedance, so at $z = 0$

$$Z_L = \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0$$

$$V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+$$

The **voltage reflection coefficient**: $\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$ (2.35)

The total voltage and current on the line:

$$V(z) = V_0^+ \left[e^{-j\beta z} + \Gamma e^{j\beta z} \right],$$

$$I(z) = \frac{V_0^+}{Z_0} \left[e^{-j\beta z} - \Gamma e^{j\beta z} \right] \quad (2.36)$$



Continued

- ❖ It is seen that the voltage and current on the line consist of a superposition of an incident and reflected wave. → *Standing waves*
- ❖ When $\Gamma = 0$ → matched.
- ❖ For the **time-average power** flow along the line at the point z :

$$\begin{aligned} P_{avg} &= \frac{1}{2} \operatorname{Re} \{ V(z) I^*(z) \} = \frac{1}{2} \frac{|V_0^+|^2}{Z_0} \operatorname{Re} \{ 1 - \Gamma^* e^{-2j\beta z} + \Gamma e^{2j\beta z} - |\Gamma|^2 \} \\ &= \frac{1}{2} \frac{|V_0^+|^2}{Z_0} (1 - |\Gamma|^2) \end{aligned}$$



Continued

- ❖ When the load is mismatched, not all of the available power from the generator is delivered to the load.
- ❖ This loss is **return loss (RL)**:

$$\mathbf{RL = -20 \log |\Gamma| \text{ dB}}$$

- ❖ If the load is matched to the line, $\Gamma = 0$ and $|V(z)| = |V_0^+|$ (constant) \rightarrow flat When the load is mismatched,

$$|V(z)| = |V_0^+| |1 + \Gamma e^{2j\beta z}| = |V_0^+| |1 + \Gamma e^{-2j\beta l}| = |V_0^+| |1 + |\Gamma| e^{j(\theta - 2\beta l)}| \quad (2.39)$$

$$V_{\max} = |V_0^+| (1 + |\Gamma|), \quad V_{\min} = |V_0^+| (1 - |\Gamma|) \quad (2.40)$$



Continued

- ❖ A measure of the mismatch of a line, called the **voltage standing wave ratio (VSWR)**

$$SWR = \frac{1+|\Gamma|}{1-|\Gamma|} \quad (1 < VSWR < \infty)$$

- ❖ From (2.39), the **distance** between 2 successive voltage maxima (or minima) is $l = 2\pi/2\beta = \lambda/2$ ($2\beta l = 2\pi$), while the distance between a maximum and a minimum is $l = \pi/2\beta = \lambda/4$.

- ❖ From (2.34) with $z = -l$,

$$\Gamma(l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \Gamma(0) e^{-2j\beta l} \quad (2.42)$$



Continued

At a distance $l = -z$,

$$Z_{in} = \frac{V(-l)}{I(-l)} = Z_0 \frac{V_0^+}{V_0^+} \left[\frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} \right] = Z_0 \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}} \quad (2.43)$$

$$\begin{aligned} &= Z_0 \frac{(Z_L + Z_0)e^{j\beta l} + (Z_L - Z_0)e^{-j\beta l}}{(Z_L + Z_0)e^{j\beta l} - (Z_L - Z_0)e^{-j\beta l}} \\ &= Z_0 \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} \\ &= Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \end{aligned} \quad (2.44)$$

→ Transmission line impedance equation



Special Cases of Terminated Transmission Lines


❖ Short-circuited line

❖ $Z_L = 0 \rightarrow \Gamma = -1$

$$V(z) = V_0^+ [e^{-j\beta z} - e^{j\beta z}] = -2jV_0^+ \sin \beta z,$$

$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} + e^{j\beta z}] = 2 \frac{V_0^+}{Z_0} \cos \beta z$$
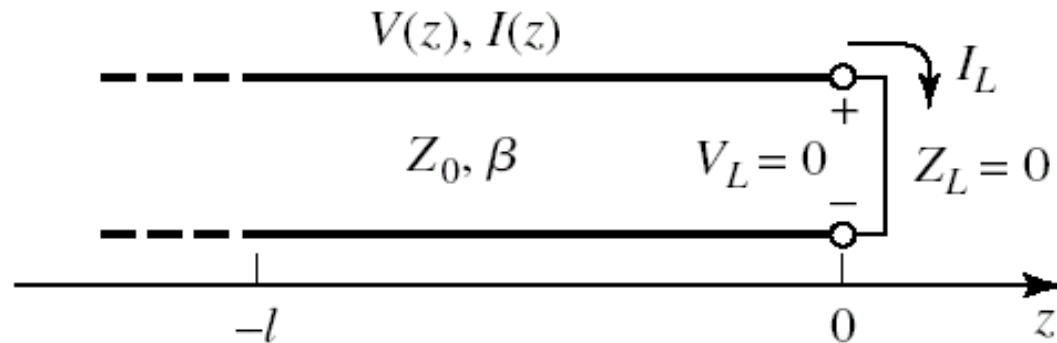
$$Z_{in} = jZ_0 \tan \beta l \quad (2.45)$$




Continued

- **Open-circuited line**

$$Z_L = \infty \rightarrow \Gamma = 1 \quad V(z) = V_0^+ [e^{-j\beta z} + e^{j\beta z}] = 2V_0^+ \cos \beta z,$$
$$I(z) = \frac{V_0^+}{Z_0} [e^{-j\beta z} - e^{j\beta z}] = \frac{-2jV_0^+}{Z_0} \sin \beta z \quad (2.46)$$

$$Z_{in} = -jZ_0 \cot \beta l$$

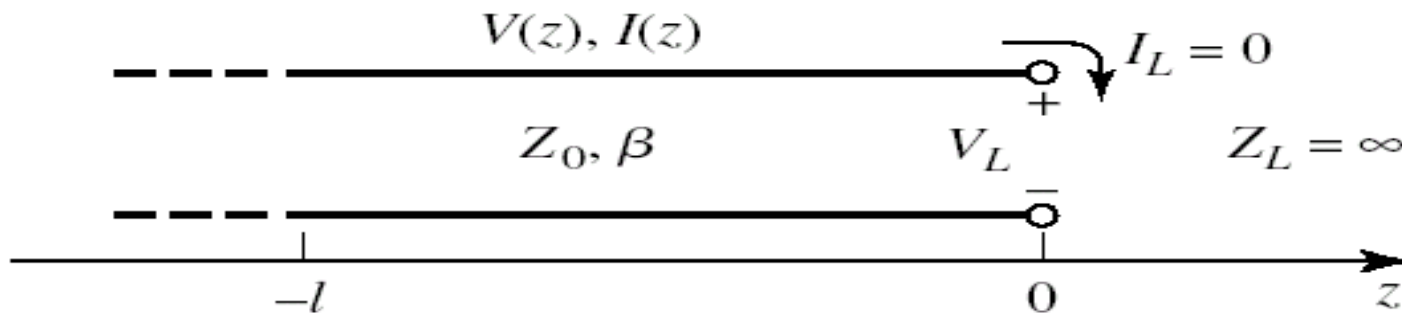

Generator and Load Mismatches

- ❖ Because both the **generator** and **load** are mismatched, multiple reflections can occur on the line.
- ❖ In the steady state, the net result is a single wave traveling toward the load, and a single reflected wave traveling toward the generator.

where $z = -l$,

$$Z_{in} = Z_0 \frac{1 + \Gamma_l e^{-2j\beta l}}{1 - \Gamma_l e^{-2j\beta l}} = Z_0 \frac{Z_l + jZ_0 \tan \beta l}{Z_0 + jZ_l \tan \beta l} \quad (2.67)$$

$$\Gamma_l = \frac{Z_l - Z_0}{Z_l + Z_0} \quad (2.68)$$



Continued

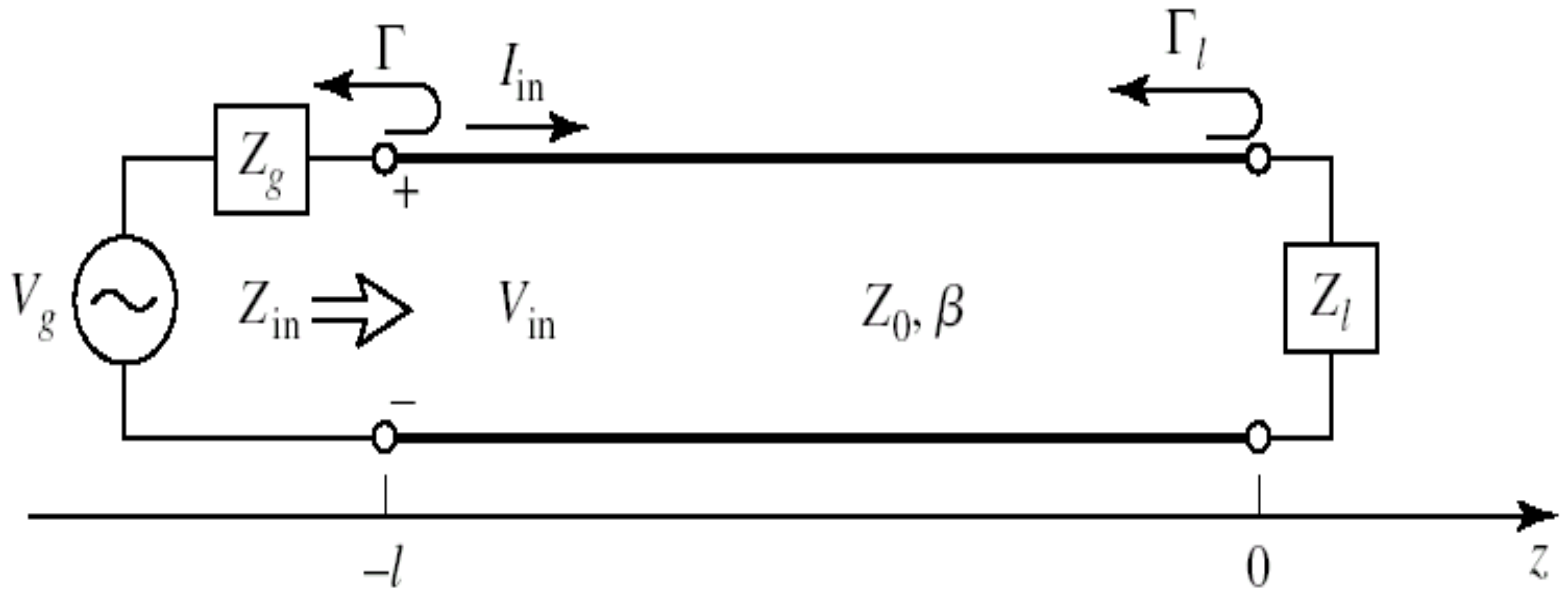


Figure 2.8 Transmission line circuit for mismatched load and generator



Continued

❖ The voltage on the line:

$$V(-l) = V_g \frac{Z_{in}}{Z_{in} + Z_g} = V_0^+ (e^{j\beta l} + \Gamma_l e^{-j\beta l})$$

$$V_0^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{e^{j\beta l} + \Gamma_l e^{-j\beta l}} \quad (2.70)$$

$$V_0^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-j\beta l}}{(1 - \Gamma_l \Gamma_g e^{-2j\beta l})} \quad (2.71)$$

By (2.67)

&

$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$$

$$SWR = \frac{1 + |\Gamma_l|}{1 - |\Gamma_l|}$$



Continued

Power delivered to the load:

$$P_l = \frac{1}{2} \operatorname{Re} \{ V_{in} I_{in}^* \} = \frac{1}{2} \operatorname{Re} \left\{ |V_{in}|^2 \frac{1}{Z_{in}^*} \right\} = \frac{1}{2} \operatorname{Re} \left\{ |V_g|^2 \left| \frac{Z_{in}}{Z_{in} + Z_g} \right|^2 \frac{1}{Z_{in}^*} \right\}$$
$$= \frac{1}{2} |V_g|^2 \frac{R_{in}}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} \quad (2.39)$$

Case 1: the load is matched to the line, $Z_l = Z_0$, $\Gamma_l = 0$, $\text{SWR} = 1$,
 $Z_{in} = Z_0$,

$$P_l = \frac{1}{2} |V_g|^2 \frac{Z_0}{(Z_0 + R_g)^2 + X_g^2} \quad (2.40)$$



Continued

❖ **Case 2:** the generator is matched to the input impedance of a transmission line, $Z_{in} = Z_g$

$$P_l = \frac{1}{2} |V_g|^2 \frac{R_g}{4(R_g^2 + X_g^2)} \quad (2.41)$$

❖ If Z_g is fixed, to maximize P_l ,

$$\frac{\partial P_l}{\partial R_{in}} = 0 \rightarrow \frac{1}{(R_{in} + R_g)^2 + (X_{in} + X_g)^2} - \frac{2R_{in}(R_{in} + R_g)}{[(R_{in} + R_g)^2 + (X_{in} + X_g)^2]^2} = 0$$



Continued

or $R_g^2 - R_{in}^2 + (X_{in} + X_g)^2 = 0$

$$\frac{\partial P_l}{\partial X_{in}} = 0 \rightarrow \frac{-2X_{in}(X_{in} + X_g)}{[(R_{in} + R_g)^2 + (X_{in} + X_g)^2]^2} = 0$$

or $X_{in}(X_{in} + X_g) = 0$

- ❖ Therefore, $R_{in} = R_g$ and $X_{in} = -X_g$, or $Z_{in} = Z_g^*$
- ❖ Under these conditions

$$P_l = \frac{1}{2} |V_g|^2 \frac{1}{4R_g} \quad (2.44)$$



Example 1

An air line has characteristic impedance of 70Ω and phase constant of 3 rad/m at 100 MHz . Calculate the inductance per meter and the capacitance per meter of the line.

Solution:

An air line can be regarded as a lossless line since $\sigma \simeq 0$. Hence

$$R = 0 = G \quad \text{and} \quad \alpha = 0$$

$$Z_0 = R_0 = \sqrt{\frac{L}{C}}$$

$$\beta = \omega \sqrt{LC}$$

$$\frac{R_0}{\beta} = \frac{1}{\omega C}$$



cont'd

$$C = \frac{\beta}{\omega R_0} = \frac{3}{2\pi \times 100 \times 10^6 (70)} = 68.2 \text{ pF/m}$$

$$L = R_0^2 C = (70)^2 (68.2 \times 10^{-12}) = 334.2 \text{ nH/m}$$

A transmission line operating at 500 MHz has $Z_0 = 80 \Omega$, $\alpha = 0.04 \text{ Np/m}$, $\beta = 1.5 \text{ rad/m}$. Find the line parameters R , L , G , and C .

Answer: $3.2 \Omega/\text{m}$, 38.2 nH/m , $5 \times 10^{-4} \text{ S/m}$, 5.97 pF/m .



Example 2

A distortionless line has $Z_0 = 60 \Omega$, $\alpha = 20 \text{ mNp/m}$, $u = 0.6c$, where c is the speed of light in a vacuum. Find R , L , G , C , and λ at 100 MHz.

Solution:

For a distortionless line,

$$RC = GL \quad \text{or} \quad G = \frac{RC}{L}$$

and hence

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\alpha = \sqrt{RG} = R \sqrt{\frac{C}{L}} = \frac{R}{Z_0}$$

$$\text{or} \quad R = \alpha Z_0$$



Cont'd

But

$$u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$R = \alpha Z_0 = (20 \times 10^{-3})(60) = 1.2 \Omega/\text{m}$$

$$L = \frac{Z_0}{u} = \frac{60}{0.6 (3 \times 10^8)} = 333 \text{ nH/m}$$

$$G = \frac{\alpha^2}{R} = \frac{400 \times 10^{-6}}{1.2} = 333 \mu\text{S/m}$$

$$uZ_0 = \frac{1}{C}$$

or

$$C = \frac{1}{uZ_0} = \frac{1}{0.6 (3 \times 10^8) 60} = 92.59 \text{ pF/m}$$

$$\lambda = \frac{u}{f} = \frac{0.6 (3 \times 10^8)}{10^8} = 1.8 \text{ m}$$



Example 3

A certain transmission line operating at $\omega = 10^6$ rad/s has $\alpha = 8$ dB/m, $\beta = 1$ rad/m, and $Z_0 = 60 + j40 \Omega$, and is 2 m long. If the line is connected to a source of $10\angle 0^\circ$ V, $Z_g = 40 \Omega$ and terminated by a load of $20 + j50 \Omega$, determine

- (a) The input impedance
- (b) The sending-end current
- (c) The current at the middle of the line



Solution:

(a) Since $1 \text{ Np} = 8.686 \text{ dB}$,

$$\alpha = \frac{8}{8.686} = 0.921 \text{ Np/m}$$

$$\gamma = \alpha + j\beta = 0.921 + j1 \text{ /m}$$

$$\gamma\ell = 2(0.921 + j1) = 1.84 + j2$$

Using the formula for $\tanh(x + jy)$, we obtain

$$\tanh \gamma\ell = 1.033 - j0.03929$$

$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{Z_L + Z_0 \tanh \gamma\ell}{Z_0 + Z_L \tanh \gamma\ell} \right) \\ &= (60 + j40) \left[\frac{20 + j50 + (60 + j40)(1.033 - j0.03929)}{60 + j40 + (20 + j50)(1.033 - j0.03929)} \right] \\ Z_{in} &= 60.25 + j38.79 \Omega \end{aligned}$$



(b) The sending-end current is $I(z = 0) = I_o$

$$\begin{aligned} I(z = 0) &= \frac{V_g}{Z_{in} + Z_g} = \frac{10}{60.25 + j38.79 + 40} \\ &= 93.03 \angle -21.15^\circ \text{ mA} \end{aligned}$$

(c) To find the current at any point, we need V_o^+ and V_o^- . But

$$I_o = I(z = 0) = 93.03 \angle -21.15^\circ \text{ mA}$$

$$V_o = Z_{in} I_o = (71.66 \angle 32.77^\circ)(0.09303 \angle -21.15^\circ) = 6.667 \angle 11.62^\circ \text{ V}$$

$$\begin{aligned} V_o^+ &= \frac{1}{2} (V_o + Z_o I_o) \\ &= \frac{1}{2} [6.667 \angle 11.62^\circ + (60 + j40)(0.09303 \angle -21.15^\circ)] = 6.687 \angle 12.08^\circ \end{aligned}$$

$$V_o^- = \frac{1}{2} (V_o - Z_o I_o) = 0.0518 \angle 260^\circ$$



At the middle of the line, $z = \ell/2$, $\gamma z = 0.921 + j1$. Hence, the current at this point is

$$\begin{aligned}
 I_s(z = \ell/2) &= \frac{V_o^+}{Z_o} e^{-\gamma z} - \frac{V_o^-}{Z_o} e^{\gamma z} \\
 &= \frac{(6.687e^{j12.08^\circ})e^{-0.921-j1}}{60 + j40} - \frac{(0.0518e^{j260^\circ})e^{0.921+j1}}{60 + j40}
 \end{aligned}$$

Note that $j1$ is in radians and is equivalent to $j57.3^\circ$. Thus,

$$\begin{aligned}
 I_s(z = \ell/2) &= \frac{6.687e^{j12.08^\circ} e^{-0.921} e^{-j57.3^\circ}}{72.1e^{j33.69^\circ}} - \frac{0.0518e^{j260^\circ} e^{0.921} e^{j57.3^\circ}}{72.1e^{j33.69^\circ}} \\
 &= 0.0369e^{-j78.91^\circ} - 0.001805e^{j283.61^\circ} \\
 &= 6.673 - j34.456 \text{ mA} \\
 &= 35.10 \angle 281^\circ \text{ mA}
 \end{aligned}$$



Example 4

A 30-m-long lossless transmission line with $Z_0 = 50 \Omega$ operating at 2 MHz is terminated with a load $Z_L = 60 + j40 \Omega$. If $u = 0.6c$ on the line, find

- (a) The reflection coefficient Γ
- (b) The standing wave ratio s
- (c) The input impedance

Solution:

This problem will be solved with and without using the Smith chart.

$$\begin{aligned} \text{(a) } \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{60 + j40 - 50}{60 + j40 + 50} = \frac{10 + j40}{110 + j40} \\ &= 0.3523 / 56^\circ \end{aligned}$$

$$\text{(b) } s = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.3523}{1 - 0.3523} = 2.088$$

$$\text{(c) Since } u = \omega/\beta, \text{ or } \beta = \omega/u,$$



$$\beta\ell = \frac{\omega\ell}{u} = \frac{2\pi(2 \times 10^6)(30)}{0.6(3 \times 10^8)} = \frac{2\pi}{3} = 120^\circ$$

Note that $\beta\ell$ is the electrical length of the line.

$$\begin{aligned} Z_{in} &= Z_0 \left[\frac{Z_L + jZ_0 \tan \beta\ell}{Z_0 + jZ_L \tan \beta\ell} \right] \\ &= \frac{50(60 + j40 + j50 \tan 120^\circ)}{[50 + j(60 + j40) \tan 120^\circ]} \\ &= \frac{50(6 + j4 - j5\sqrt{3})}{(5 + 4\sqrt{3} - j6\sqrt{3})} = 24.01 \angle 3.22^\circ \\ &= 23.97 + j1.35 \Omega \end{aligned}$$

