

Chapter 4&5: Passive and Active Microwave Devices and Networks

**Good
Morning**



Sem. II, Year IV

Microwave Devices and Systems

By Waltengus A

Outline

- ❖ **Basic principles of passive and active microwave devices**
- ❖ **Types of passive and active microwave devices**
- ❖ **Matching network design**

Passive Devices

- ❖ Maxwell's equations govern all types of electromagnetic behavior at all frequencies.
- ❖ At lower frequencies (below about 500 MHz) where lumped components are less than $\lambda/8$ in length, it is convenient to define the component as a frequency-independent R, L, or C.
- ❖ As the frequency increases, the component will have distributed effects or added phase shift which must be accounted for in the analysis.
- ❖ As electrical engineers, we first learn to analyze lumped-element circuits consisting of R, L, and C components, which are independent of frequency; the impedance or admittance of the components is linearly dependent on frequency.
- ❖ Then we learn that at high frequencies additional parasitic effects must be included in the model of the component.

.....Con'td

- ❖ For lumped components at low frequencies signals travel at essentially the speed of light instantaneously through points in space where the component is located.
- ❖ At microwaves (defined as 300 MHz to 30 GHz, with above 30 GHz also called **millimeter wave**), the electrical component used to generate and process signals has a size similar to an eighth of a wavelength.
- ❖ Then we must back up to Maxwell's equations subject to the appropriate boundary conditions.

Chip Resistor Versus Size and Typical Parasitic C and L

Resistor Size	Length (mm)	Width (mm)	Capacitance (pF)	Inductance (nH)
1206	3.2	1.6	0.05	2
0805	2.0	1.25	0.09	1
0603	1.6	0.8	0.05	0.4
0402	0.5	0.5		

Active Devices

- ❖ **The majority of microwave circuits use active devices one way or another.**
- ❖ **While some applications operate the devices in a linear range, many applications need to understand the behavior under large-signal conditions.**
- ❖ **Typical examples for large signal operations are mixer and oscillator circuits as well as power amplifiers.**

- ❖ **The basic nonlinearities are frequency independent, and yet because the nonlinear capacitance of the device starts playing a major role at higher frequencies, their effect has to be considered.**

.....Con'td

- ✓ This chapter will provide some high-frequency insight into the commonly used **microwave active devices** and prepare the reader for large-signal considerations.
- ✓ This chapter begins with a detailed discussion of diode nonlinear performance, including: the pn junction, the Schottky diode, the pin diode, and the varactor diode (variable reactance).
- ✓ The basic nonlinearities are the capacitance and the forward bias current.
- ✓ Next the many forms of three-terminal transistors will be covered:

- ❖ **BJT** A current controlled transistor which is a minority carrier device in the base region; this a bipolar device because there are **two junctions**, the **emitter–base junction**, which is forward biased to inject the minority carriers into the **base**, and the **collector–base junction**, which is reverse biased to collect all of the base minority carriers into the **collector**.
- ❖ **MOSFET** Modern metal–oxide–semiconductor field-effect transistors (MOSFETs) have become important at frequencies below 2.5 GHz.
- ✓ The nonlinear models come from SPICE developments, including bipolar CMOS nonlinear (Bi-CMOS) models among others.
- ✓ Bi-CMOS implies that BJTs, n-channel MOSFETs, and p-channel MOSFETs are on the same silicon chip.

.....Con'td

- ❖ **MESFET:** This transistor came about in 1965 with the development of Schottky diodes and ohmic contacts simultaneously on GaAs.
 - ✓ It is a majority-carrier device which is voltage controlled at the gate. The name means metal–semiconductor field-effect transistor.
- ❖ **HEMT:** (PHEMT and MHEMT) This is replacing MESFETs in many applications due to superior performance.
 - ✓ It is a high-electron-mobility transistor first introduced about 1980 by Fujitsu. It has progressed to PHEMT and MHEMT structures, with even better performance.
 - ✓ A PHEMT is a lattice-matched pseudo morphic HEMT, while a MHEMT is a metamorphic HEMT, a newer development with great promise, where graded layers of doping are employed.
- ❖ **HBT:** The hetero junction bipolar transistor (HBT) was originally developed to improve emitter injection efficiency in GaAs BJTs, which has been a longstanding problem (since 1965).

.....Con'td

Six Active Device Types

BJT	MOSFET	MESFET	PHEMT	MHEMT	HBT
Ge	CMOS	Si	Al ₂ O ₃ GaAs	InAlAs/InGaAs	InGaP/InGaAs
Si	DMOS LDMOS	GaAs	InGaAs		SiGe

- ❖ Some recent developments include the enhancement- as well as depletion-mode PHEMTs, which are serious contenders for 2-GHz wireless amplifiers.
- ❖ The newer materials being developed today offer even further improvements in the near future, such as SiC and GaN, very promising high-power FETs.
- ❖ In addition n-channel MOSFETs have shown considerable promise at 60 GHz.

- ❖ In designing a **microwave circuit**, which will be built on a material such as GaAs, one needs to go to a GaAs alternative silicon or silicon germanium foundry.
- ❖ The foundries seem to be very secretive about their information, and the first experience with a foundry is a shock because one needs to sign a nondisclosure agreement and pay up to \$5000 to obtain a foundry manual.
- ❖ These foundry manuals are somewhat unique to each foundry and vary.
- ❖ The foundry supplies information about **passive** and **active** structures as well as interconnect information.

- ❖ The following is an example of foundry manual which was put together from information from various foundries.
- ❖ It does not apply to a particular foundry but is generic in its contents. In the area of passive components, typically a variety of inductor cells are recommended: the same applies to spiral inductors/rectangular inductors and interconnect components such as bends, tees, crosses, and other components as outlined.

Active Versus Passive Devices

An **active device** is any type of circuit component with the ability to electrically control electron flow (electricity, controlling electricity).

- ❖ A circuit to be properly called *electronic*, it must contain at least one active device.
- ❖ Active devices include, but are not limited to, vacuum tubes, transistors, silicon-controlled rectifiers (SCRs)
- ❖ Components incapable of controlling current by means of another electrical signal are called **passive devices**. Resistors, capacitors, inductors, transformers, and even diodes are all considered passive devices.

- ❖ **All active devices control the flow of electrons through them.**
- ❖ **Some active devices allow a voltage to control this current while other active devices allow another current to do the job.**
- ❖ **Devices utilizing a static voltage as the controlling signal are, not surprisingly, called *voltage-controlled devices*.**
- ❖ **Devices working on the principle of one current controlling another current are known as *current-controlled devices*.**
- ❖ **For the record, vacuum tubes are voltage-controlled devices while transistors are made as either voltage-controlled or current controlled types.**
- ❖ **The first type of transistor successfully demonstrated was a current-controlled device.**

- ❖ Basic and vague difference is **active devices** are made of active elements like OPAMPS, CMOS,BJTs etc. while passive devices are made of passive elements like resistors etc.
- ❖ Passive elements **looses power** like resistor provides a voltage drop across it whereas active elements have **low power** dissipation like current mirrors.
- ❖ Active Elements have **low dynamic** and **static power losses** and are **highly efficient** than passive elements.
- ❖ Passive devices never provide gain. You cannot get an amplified wave after passing through a passive network.
- ❖ Active Devices are more **superior** and efficient than Passive Devices.
- ❖ Active device is one which **doesn't required external energy** to perform prescribed task while Passive device required external energy.
- ❖ Active devices are **self generating devices**.

Active Components

- ❖ Any component that is capable of providing a power gain is called an **active component**.
- ❖ They inject power to the circuit, and can control the current (or energy) flow within the circuit.
- ❖ Any electronic circuit should contain at least one **active component to operate**.
- ❖ Some examples for active devices are **battery, vacuum tubes, transistor and SCR (silicon controlled rectifier / thyristor)**.
- ❖ Controlling the current flow in circuit may be helped by another small current or voltage.
- ❖ They are called **current controlled devices** (ex: **Bipolar Junction Transistor**) and **voltage controlled devices** (example **Field Effect Transistor**).

Passive Components

- ❖ Components that cannot provide any power gain to the circuit are called **passive devices**.
- ❖ These devices are incapable of controlling the current (energy) flow in the circuit and need the help of **active devices to operate**.
- ❖ Some examples for passive devices are **resistors, inductors and capacitors**.
- ❖ Although passive components cannot amplify a signal with a gain more than one, they can multiply a signal by a value less than one.
- ❖ They also can oscillate, phase shift and filter signals.
- ❖ Some passive components also have the capability to store energy (drawn from an active element) and release later.
- ❖ Example: capacitors and inductors.

Impedance Matching

- ❖ Impedance matching is a vitally important part of **amplifier design**. There are **four main** reasons for impedance matching:
- ✓ To match an impedance to the conjugate impedance of a source or load for **maximum power transfer**
- ✓ To match an amplifier to a certain load value to provide a required **transistor gain**
- ✓ To match an amplifier to a load that does **not cause transistor instability**.
- ✓ To provide a load for an oscillator that will **cause instability and hence oscillations**.

Matching methods

There are many means of impedance matching. These include:

- ❖ **Quarter wave transmission line matching**
- ❖ **Capacitive matching**
- ❖ **Single stub matching**
- ❖ **L- network matching**
- ❖ **Double stub matching**
- ❖ **Pi- network matching**
- ❖ **Transformer matching**
- ❖ **T- network matching**
- ❖ **Auto-transformer matching**

Objectives of Smith charts

- ❖ Evaluate impedance and admittance networks;
- ❖ Design impedance and admittance networks;
- ❖ Design matching networks.
- ❖ Understand scattering parameters;
- ❖ Use two port scattering parameters efficiently;
- ❖ Design two port scattering networks;
- ❖ Evaluate two port scattering networks;
- ❖ Calculate the frequency response of networks;
- ❖ Calculate the gain of two port networks or an amplifier;
- ❖ Calculate the input impedance of two port networks or an amplifier,
- ❖ Manipulate two port data into other types of parameter data.

Smith Chart

- ❖ The Smith Chart is a **clever tool** for analyzing transmission lines
- ❖ The outside of the chart shows location on the **line in wave lengths.**
- ❖ The combination of intersecting circles inside the chart allow us to locate the normalized impedance and then to find the **impedance anywhere on the line.**
- ❖ Thus, the **first step** in analyzing a transmission line is to locate the **normalized load impedance** on the chart.
- ❖ Next, a circle is drawn that represents the **reflection coefficient** or **Standing wave ratio (SWR).**

- ❖ The center of the circle is the **center of the chart**.
- ❖ The circle passes through the **normalized load impedance**
- ❖ Any point on the line is found on this circle.
- ❖ Rotate **clockwise** to move toward the generator (away from the load)
- ❖ The distance moved on the **line** is indicated on the outside of the chart in **wavelengths**


To ward
Generator

Constant
Reflection
Coefficient Circle

Away From
Generator

Scale in
Wavelengths

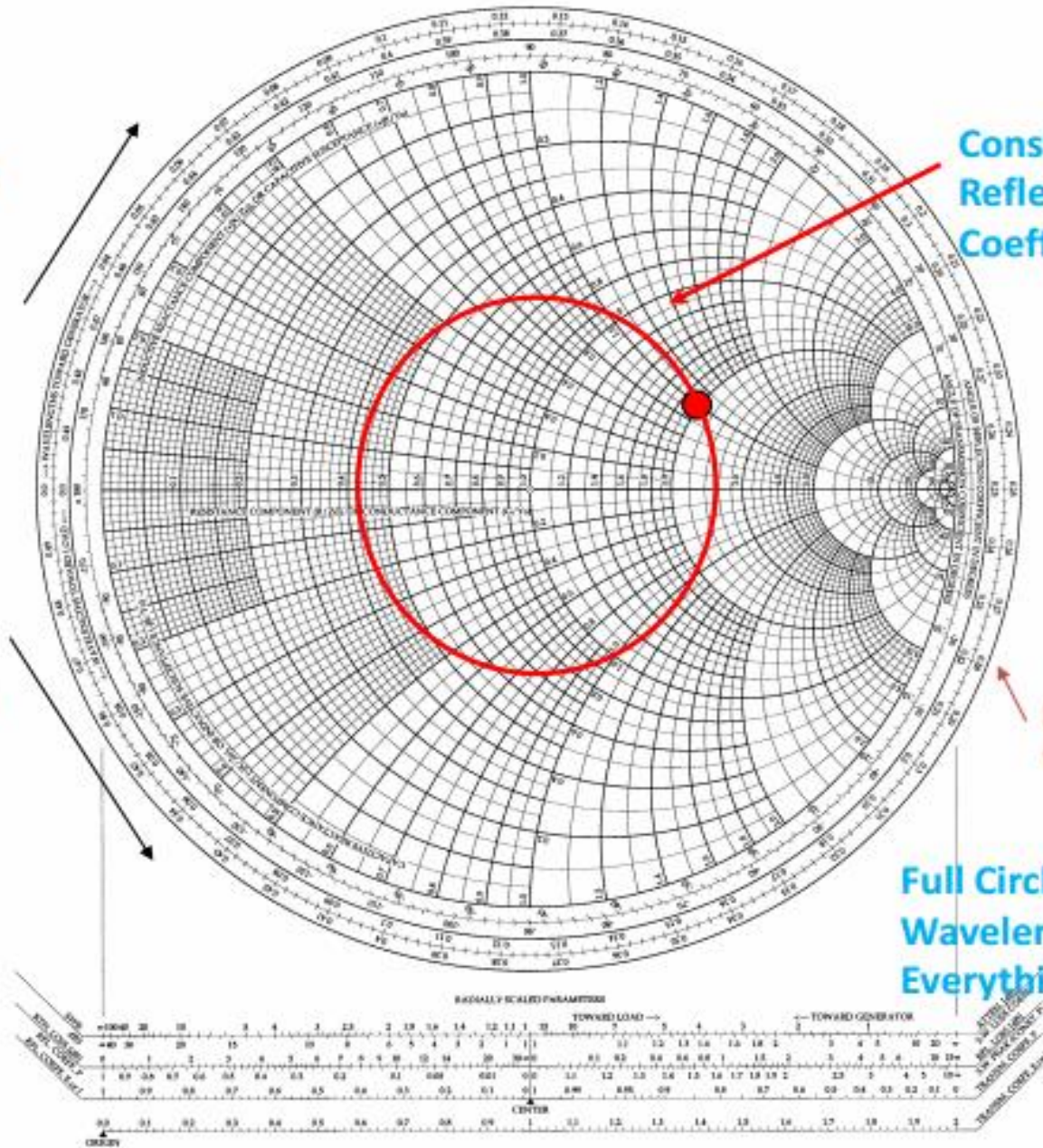Full Circle is One Half
Wavelength Since
Everything Repeats



Impedance divided by line impedance (50 Ohms)

$$Z1 = 100 + j50$$

$$Z2 = 75 - j100$$

$$Z3 = j200$$

$$Z4 = 150$$

$$Z5 = \text{infinity (an open circuit)}$$

$$Z6 = 0 \text{ (a short circuit)}$$

$$Z7 = 50$$

$$Z8 = 184 - j900$$

Then, normalize and plot. The points
are plotted as follows:

$$Z1 = 2 + j$$

$$Z2 = 1.5 - j2$$

$$Z3 = j4$$


$$Z4 = 3$$

$$Z5 = \text{infinity}$$

$$Z6 = 0$$

$$Z7 = 1$$

$$Z8 = 3.68 - j18$$

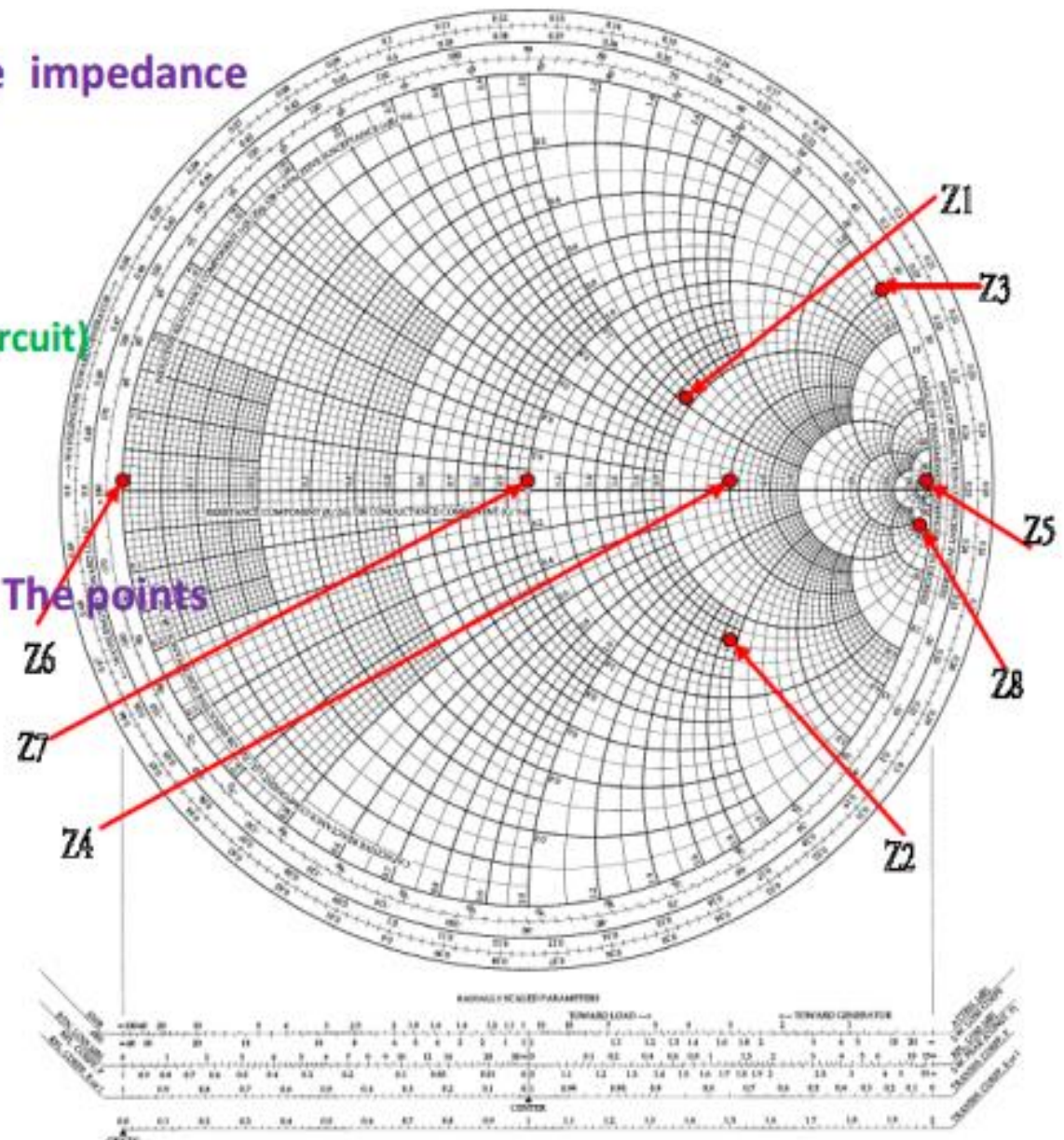

The Smith chart is the representation in the reflection coefficient plane, called the Γ plane, of the relation

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

for all values of Z , such that $\text{Re}[Z] \geq 0$. Z_0 is the characteristic impedance of the transmission line or a reference impedance value. Defining the normalized impedance z as $z = Z/Z_0$,

$$\Gamma = \frac{z - 1}{z + 1}$$

Impedances having a negative real part will have a reflection coefficient whose magnitude is greater than 1. These impedances, therefore, map outside the Smith chart.

An alternative way of handling negative resistances (i.e., $|\Gamma| > 1$) is to plot in the Smith chart $1/\Gamma^*$ and take the values of the resistance circles as being negative and the reactance circles as labeled.

Example


Find the impedance whose reflection coefficient is $2.236e^{j26.56^\circ}$.

Solution. we plot in the Smith chart

$$\frac{1}{\Gamma^*} = 0.447e^{j26.56^\circ}$$

the resulting z is $-2 + j1$.
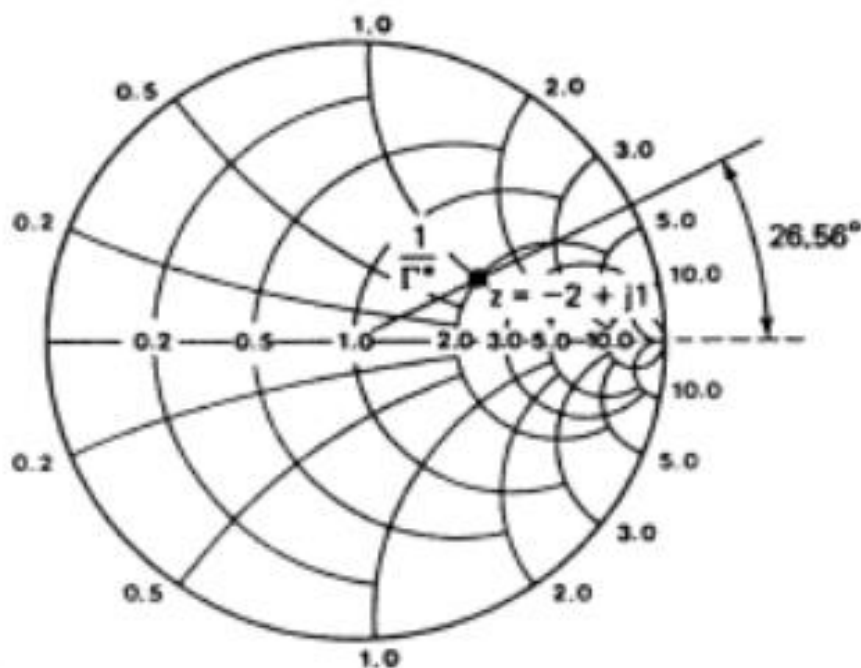
$$\Gamma = \frac{-2 + j1 - 1}{-2 + j1 + 1} = 2.236e^{j26.56^\circ}$$



For a lossless transmission line,

$$\Gamma_0 = \frac{z - 1}{z + 1}$$


$$\Gamma_{\text{IN}}(d) = \Gamma_0 e^{-j2\beta d}$$

$$z_{\text{IN}}(d) = \frac{1 + \Gamma_{\text{IN}}(d)}{1 - \Gamma_{\text{IN}}(d)}$$

A typical transmission-line input impedance calculation involves the following steps:

1. Locate Γ_0 in the Z Smith chart for a given $z = Z_L/Z_0$.
2. Rotate Γ_0 by $-2\beta d$ to obtain $\Gamma_{\text{IN}}(d)$. Observe that the rotation is along a vector of constant magnitude, namely $|\Gamma_0| = |\Gamma_{\text{IN}}(d)|$.
3. Read the value of the normalized $z_{\text{IN}}(d)$ associated with $\Gamma_{\text{IN}}(d)$

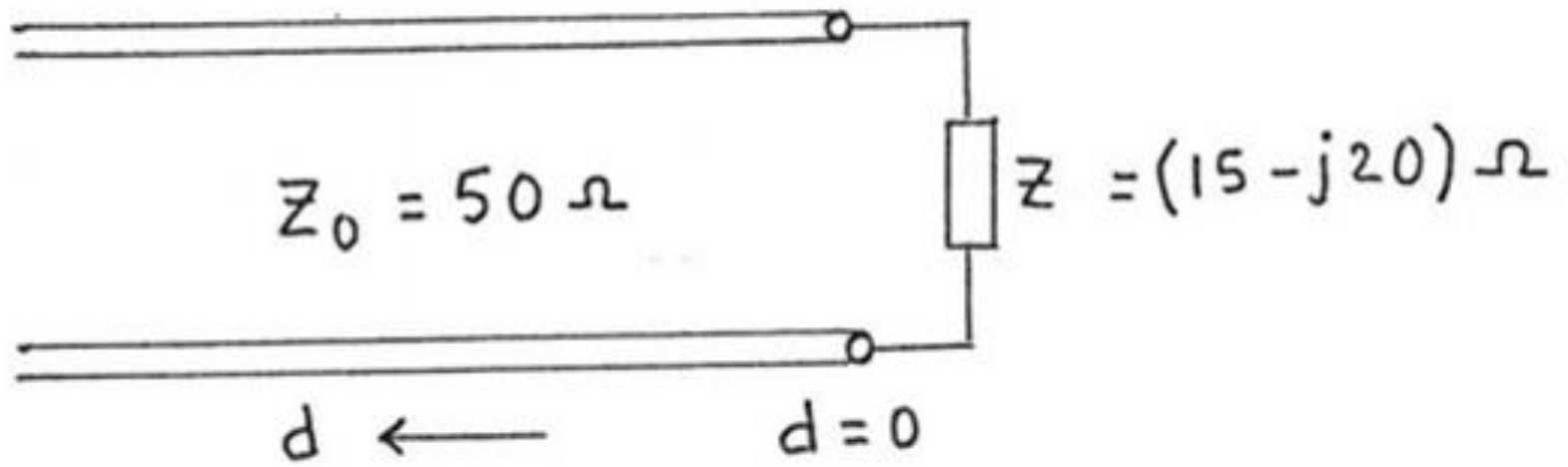Determination of Standing Wave Parameters



$$\bar{\Gamma} = \frac{Z}{Z_0} = \frac{15 - j20}{50} = 0.3 - j0.4$$

- 1) Locate $\bar{\Gamma}$ ($= 0.3 - j0.4$) at point A.
- 2) Measure $|OA|$ relative to the radius of the chart, and $\angle OA$.

$$\bar{\Gamma} = 0.6 \angle -133^\circ$$

- 3) Draw constant SWR circle through point A and locate V_{\max} point at point B.


4) Read r value at point B.

$$SWR = r_{\max} = 4.0$$

5) Locate V_{\min} point at point C
on the constant SWR circle.

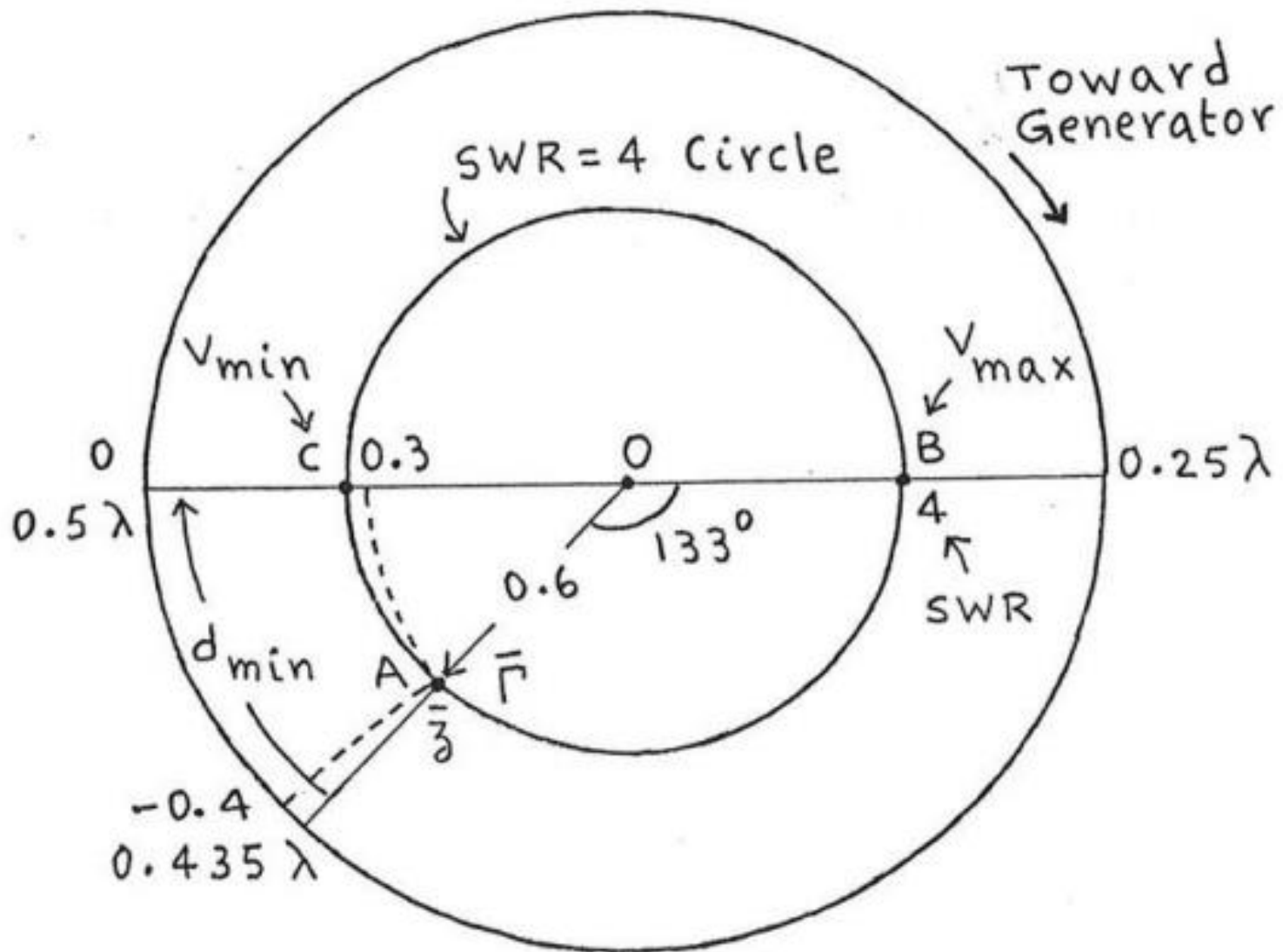
6) Find distance from A to C
toward generator.

$$\begin{aligned} d_{\min} &= (0.5 - 0.435) \lambda \\ &= 0.065 \lambda \end{aligned}$$











Why matching is important?

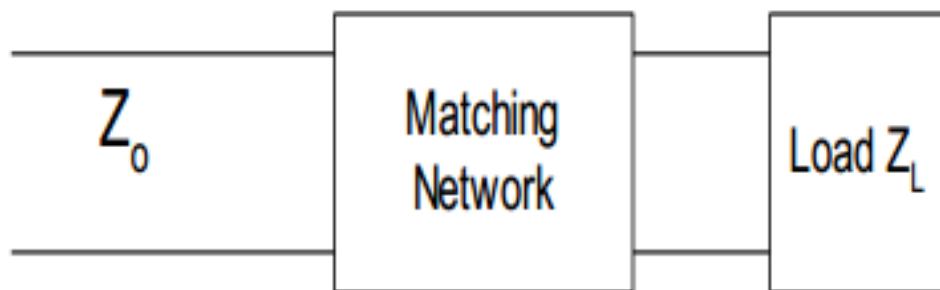- ❖ **To maximize power delivery and minimize power loss**
- ❖ **To improve signal to noise ratio as in sensitive receiver components**
- ❖ **To reduce amplitude and phase error**



Factors in selecting matching network


- ❖ **Complexity:** simpler, cheaper, more reliable and low loss circuit is preferred.
- ❖ **Bandwidth:** match over a desirable bandwidth.
- ❖ **Implementation:** depend on types of transmission line either cable, stripline, microstripline, waveguide, lump circuit etc.
- ❖ **Adjustability:** some network may need adjustment to match a variable load.
- ❖ The **Smith Chart** can be used to design a **lumped (L-C)** matching network **to match one impedance to another**
- ❖ Each LC element behaves in a certain way on the chart

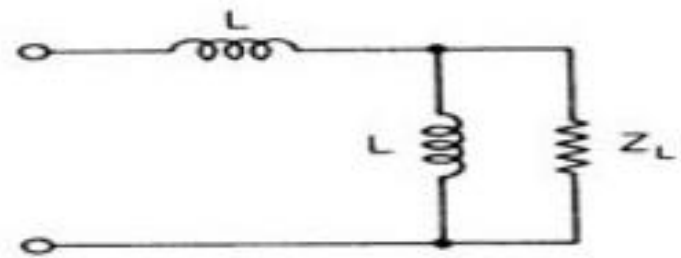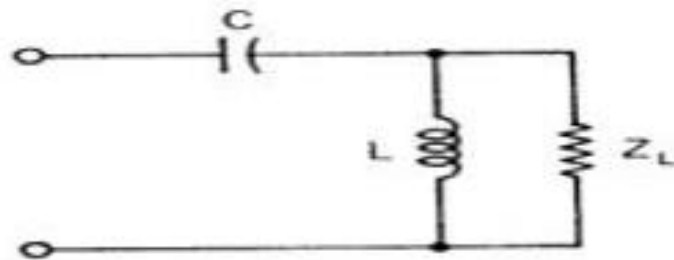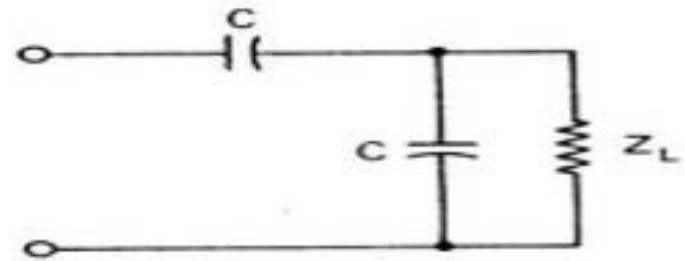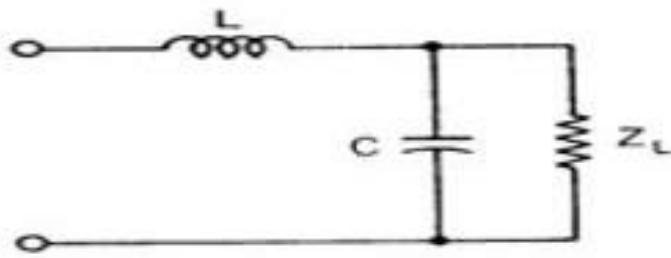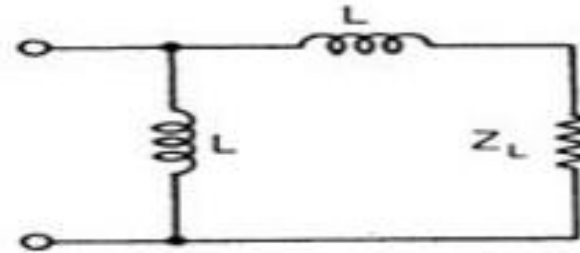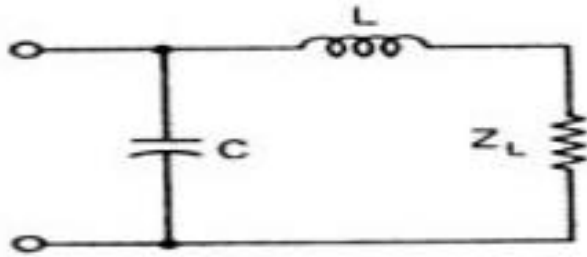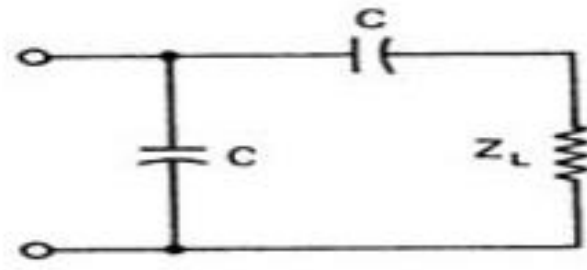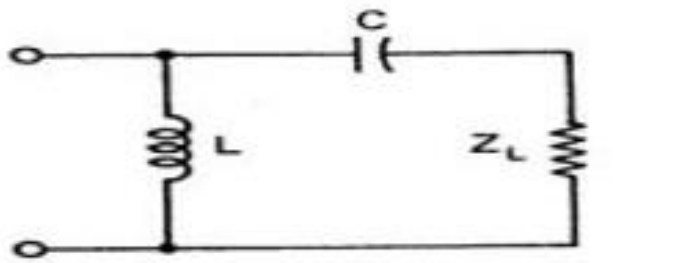

Matching networks.

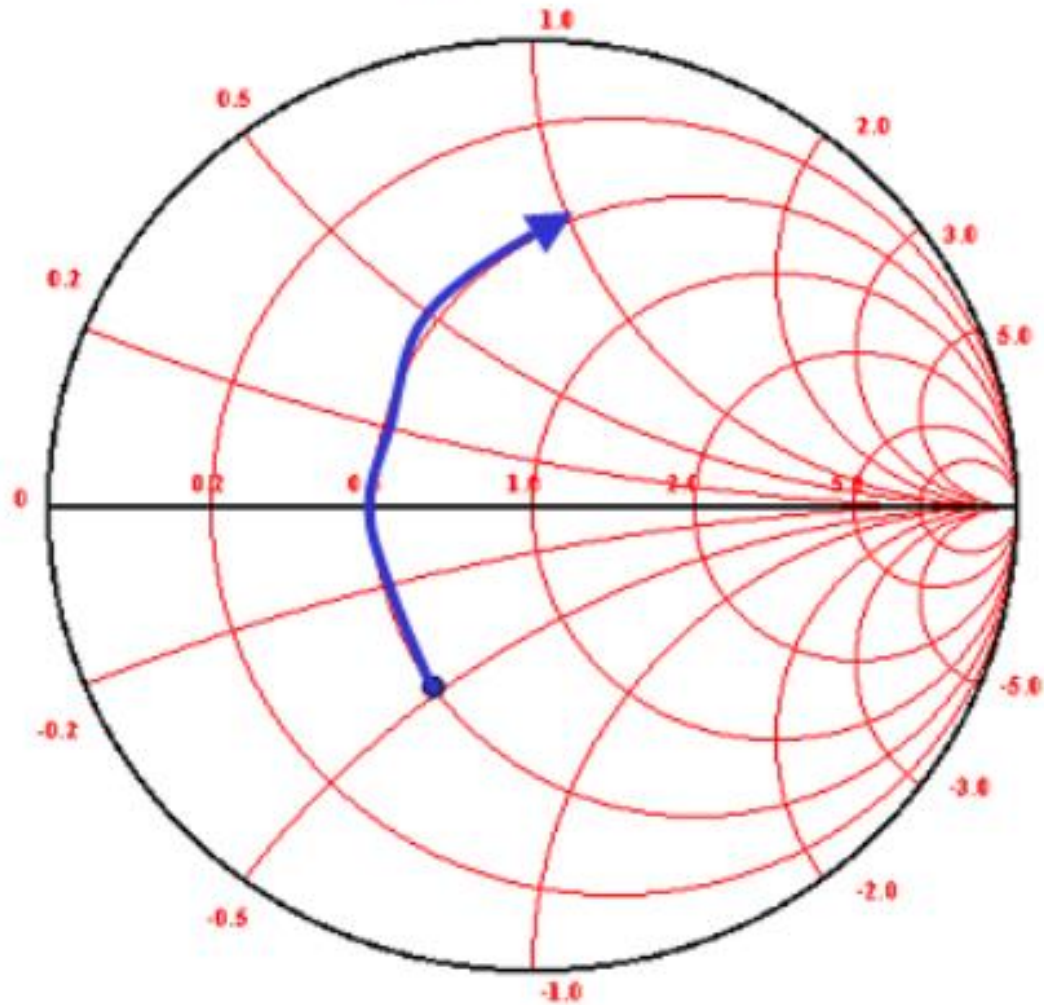
1. Series Inductors

❖ Moves clockwise along circles of constant resistance



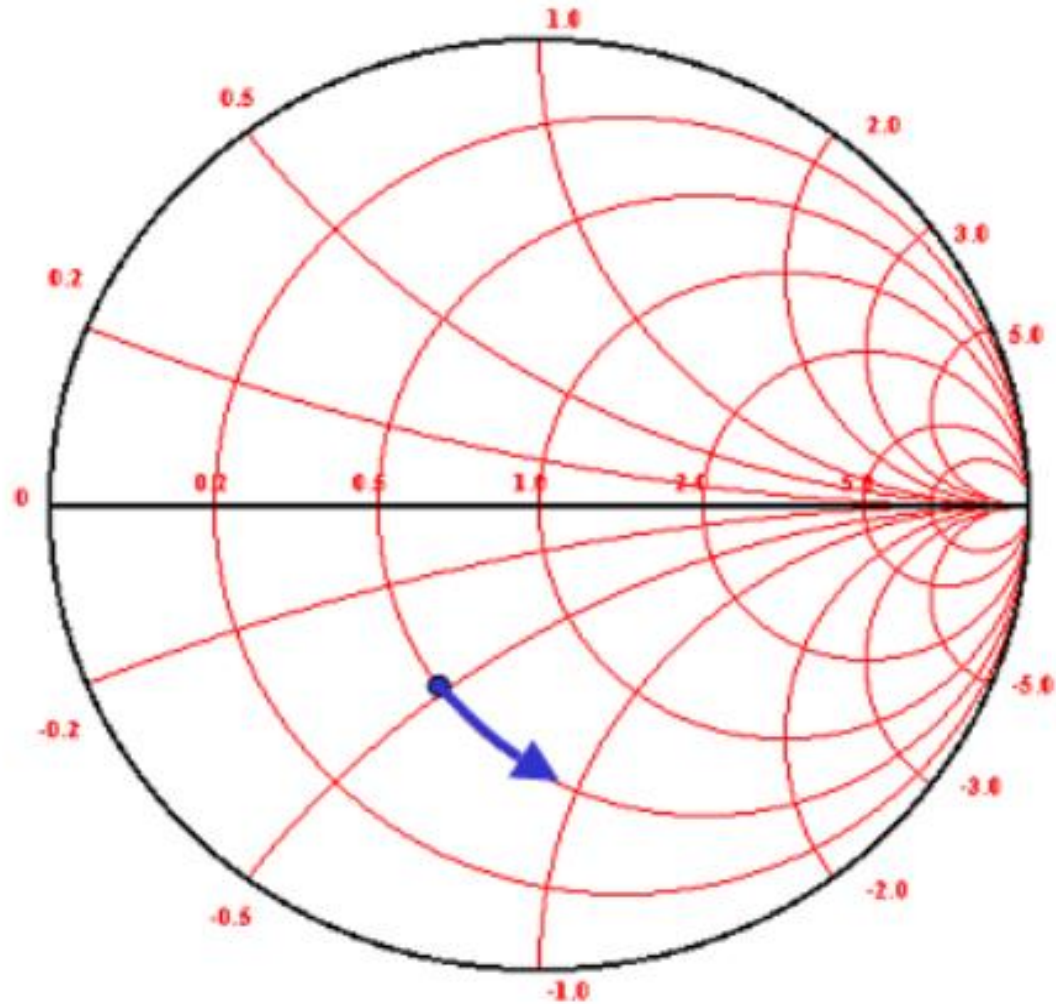
2. Series Capacitors

- ❖ Moves counter-clockwise along circles of constant resistance



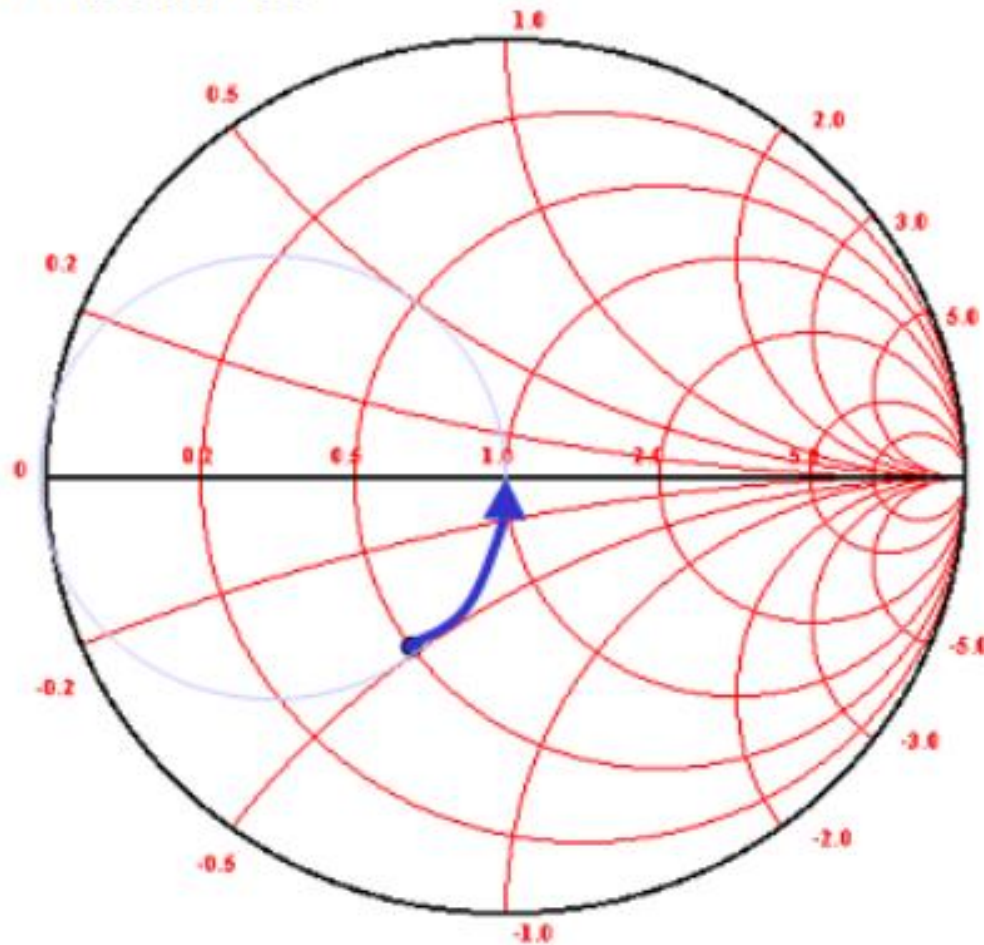
3. Shunt Inductors

- ❖ Moves counter-clockwise along circles of constant conductance



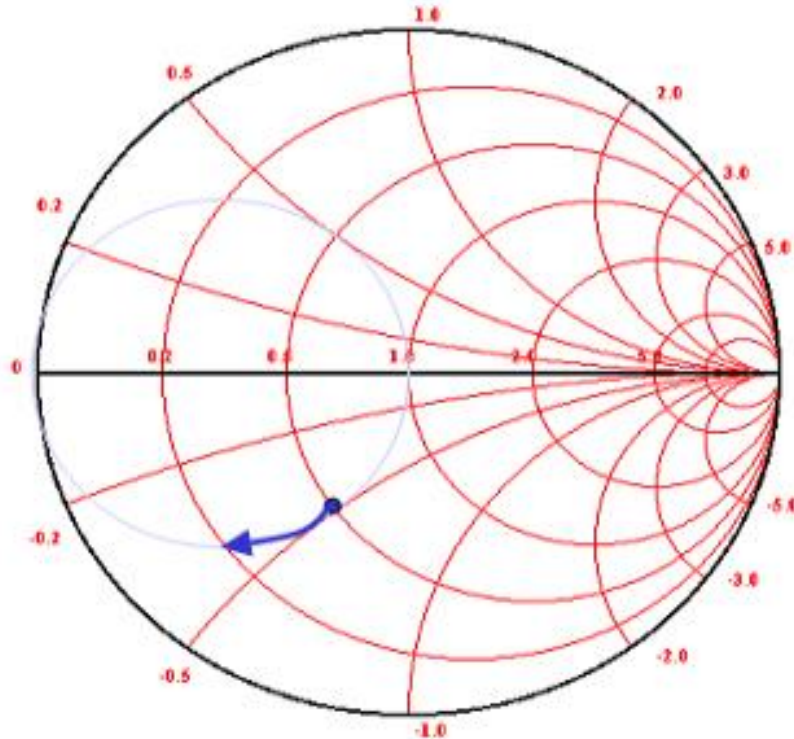4. Shunt Capacitors

- ❖ Moves clockwise along circles of constant conductance



Smith chart applications

- ❖ To find reflection coefficients and
- ❖ Impedances of networks.

Questions ?



Thanks !!!